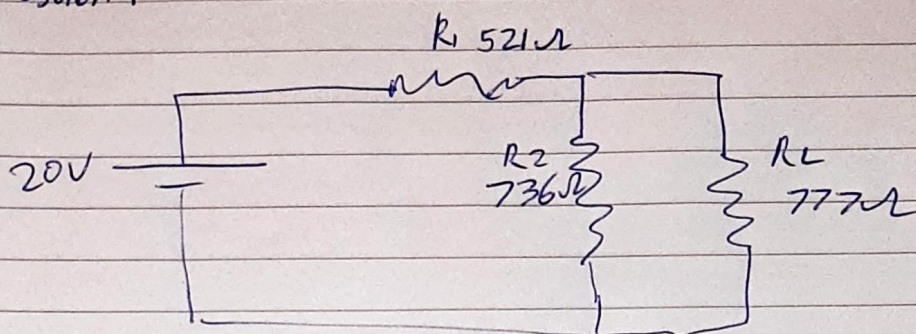


21236277

Question 1

a)



$$R_1 = 500 + 21 = 521\Omega$$

$$R_2 = 500 + 236 = 736\Omega$$

$$R_L = 500 + 277 = 777\Omega$$

$$\frac{1}{R_{||}} = \frac{1}{736} + \frac{1}{777}$$

$$R_{||} = 377,97$$

$$R_T = 377,97 + 521 = 898,97\Omega$$

$$V_T = I_T \cdot R_T$$

$$20 = I_T \cdot 898,97$$

$$I_T = 0,02224A = 22,24mA$$

$$I_1 = I_T = 0,02224A = 22,24mA$$

R_1

$$I = 0,02224$$

$$R = 521$$

P

$$P = \sqrt{VI}$$

$$P_{R_1} = 11,59 \times 0,0224$$

$$= 0,25961W$$

$$= 259,61mW$$

$$V = I \cdot R$$

$$V = 11,59V$$

$$V_{R_1} + V_{R_{||}} = V_S$$

$$11,59 + V_{R_{||}} = 20$$

$$V_{R_{||}} = 8,41$$

$$\therefore V_{R_2} = V_{R_L} = 8,41V \rightarrow$$

R₂

$$V = 8,41V$$

$$R = 736\Omega$$

$$V = I \cdot R$$

$$I_2 = \frac{8,41}{736} = 0,01142A$$

$$= 11,42mA \rightarrow$$

$$P = V \cdot I$$

$$= 8,41 \times 0,01142$$

$$= 0,09604W$$

$$= 96,04mW \rightarrow$$

R_L

$$V = 8,41V \rightarrow$$

$$R = 777\Omega$$

$$P = \frac{V^2}{R} = 0,09102W = 91,02mW \rightarrow$$

$$\cancel{I_T = I_2 + I_3} \quad I_T = I_2 + I_3$$

$$0,02224 = 0,01142 + I_3$$

$$I_3 = 0,01082A = 10,82mA \rightarrow$$

$$P_T = V_T \cdot I_T$$

$$P_T = 20 \cdot (0,02224)$$

$$P_T = 0,4448W$$

$$P_T = 444,80mW \rightarrow$$

b) $3.6V$ $t?$
 $20kJ$

i. $100mA$


ii. $200mA$

$$P = \frac{W}{t}$$

i) $P = VI$
 $= (3.6)(0.1)$
 $= 0.36W$

$$P = \frac{W}{t}$$

$$0.36 = \frac{20000}{t}$$

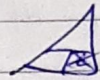

$$t = \frac{20000}{0.36}$$

$$t = 55555.55556 \text{ seconds}$$


$$t = 15.43 \text{ hours}$$

ii) $P = \frac{W}{t}$

$$t = \frac{20000}{0.36 \times 2} = 27777.77778 \text{ seconds}$$

$$= 7.72 \text{ hours}$$

c)

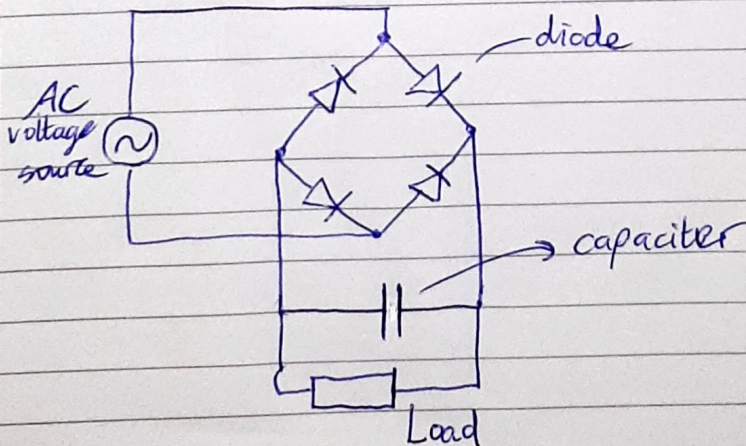

c) description of components:

Capacitor: slowly charges and releases energy which smooths out the waveform to ~~look~~ be closer to the fixed waveform of DC current.


diodes only allow current to pass in one direction. Their arrangement provides voltage to output for both ~~half~~ halves of the AC cycle.

AC ~~p~~ voltage source - supply power

load - a resistor to watch the ~~ff~~ effect of rectification.

Question 2

a) i.

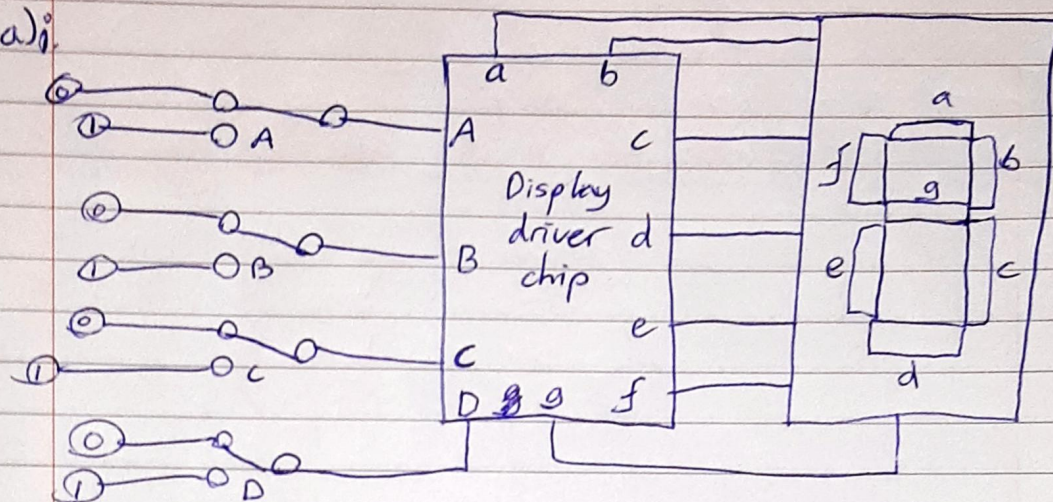

ii.

Decimal	A	B	C	D	a	f
0	0	0	0	0	1	1
1	0	0	0	1	0	0
2	0	0	1	0	1	0
3	0	0	1	1	1	0
4	0	1	0	0	0	1
5	0	1	0	1	1	1
6	0	1	1	0	1	1
7	0	1	1	1	1	0
8	1	0	0	0	1	1
9	1	0	0	1	1	1
10	1	0	1	0	X	X
11	1	0	1	1	X	X
12	1	1	0	0	X	X
13	1	1	0	1	X	X
14	1	1	1	0	X	X
15	1	1	1	1	X	X

a)

iii.

ABCD

~~000~~ ~~000~~ 0010 should have a "1" in it in the Karnaugh map to represent a. In the Karnaugh map there is a "0" at 0010, so it represents f.

		CD			
		00	01	11	10
AB	00	1	0	0	0
	01	1	1	0	1
	11	x	x	x	x
	10	1	1	x	x

group 1

~~0000~~
0000
0100
1000
 $\bar{C}\bar{D}$

group 3

0110
1110
BCD

group 2


1000
1001
 $A\bar{B}\bar{C}$

group 3

~~0100~~
0101
1100
1101
 $B\bar{C}$

$$f = C'.D' + A.B'.C' + B.C' + B.C.D'$$

iv.

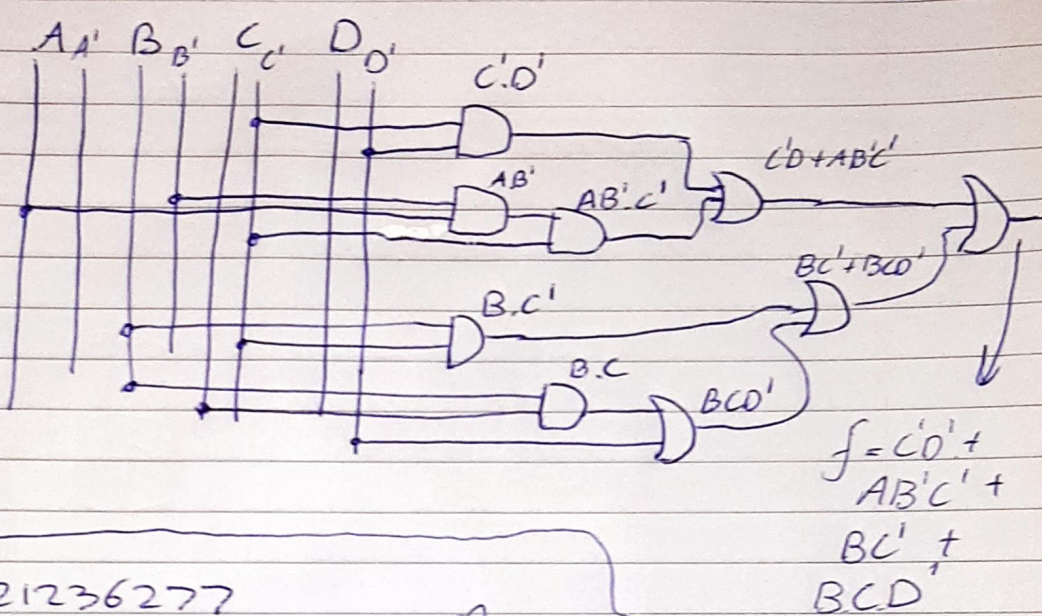

b).

- 21236277
- $\div 2 = 1061838 + 1$
 - $\div 2 = 530919 + 0$
 - $\div 2 = 265459 + 1$
 - $\div 2 = 132729 + 1$
 - $\div 2 = 66364 + 1$
 - $\div 2 = 33182 + 0$
 - $\div 2 = 16591 + 0$
 - $\div 2 = 8295 + 1$
 - $\div 2 = 4147 + 1$
 - $\div 2 = 2073 + 1$
 - $\div 2 = 1036 + 1$
 - $\div 2 = 518 + 0$
 - $\div 2 = 259 + 0$
 - $\div 2 = 129 + 1$
 - $\div 2 = 64 + 1$
 - $\div 2 = 32 + 0$
 - $\div 2 = 16 + 0$
 - $\div 2 = 8 + 0$
 - $\div 2 = 4 + 0$
 - $\div 2 = 2 + 0$
 - $\div 2 = 1 + 1$

answer: 10000

0110011
110011101

c).